

NEC芯片原理图—用78K0/78K0S来控制电熨斗

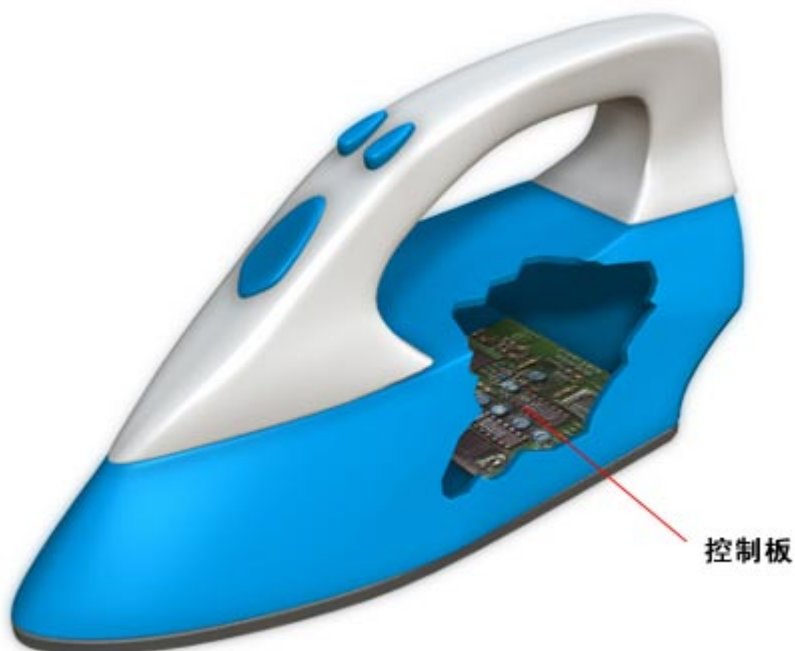


图 (1)

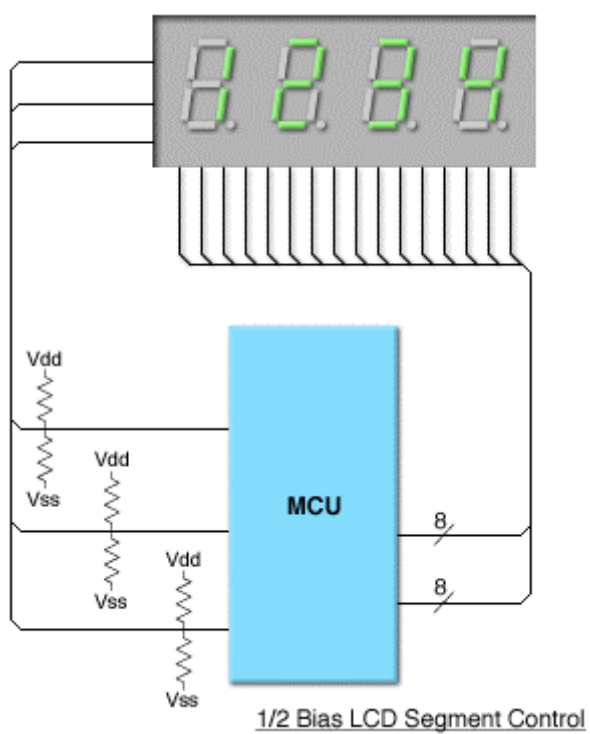


图 (2)

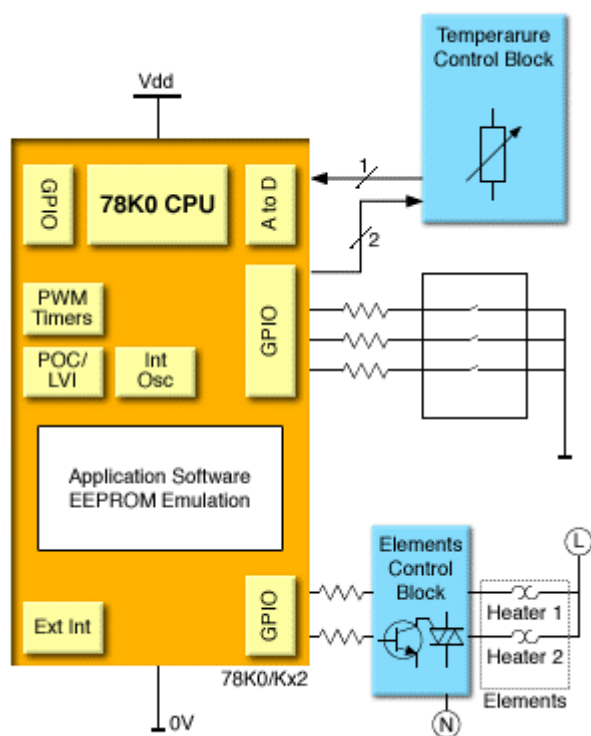


图 (3)