

## NEC芯片原理图一用78K0/78K0S来控制冰箱

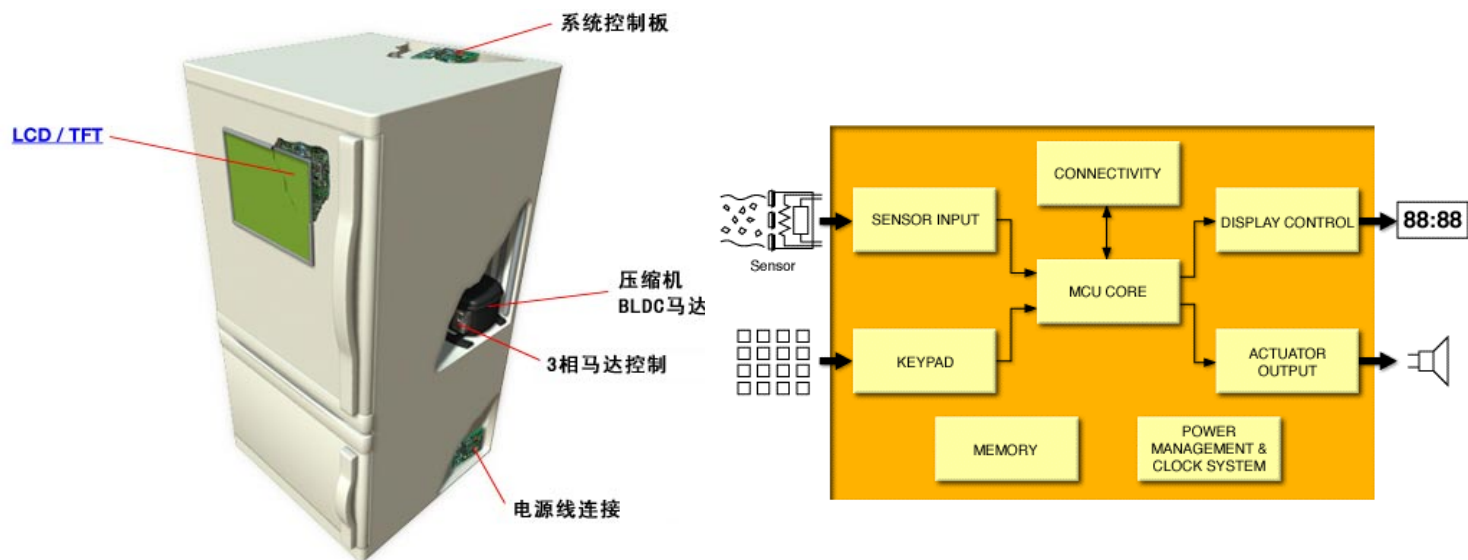


图 (1)

图 (2)

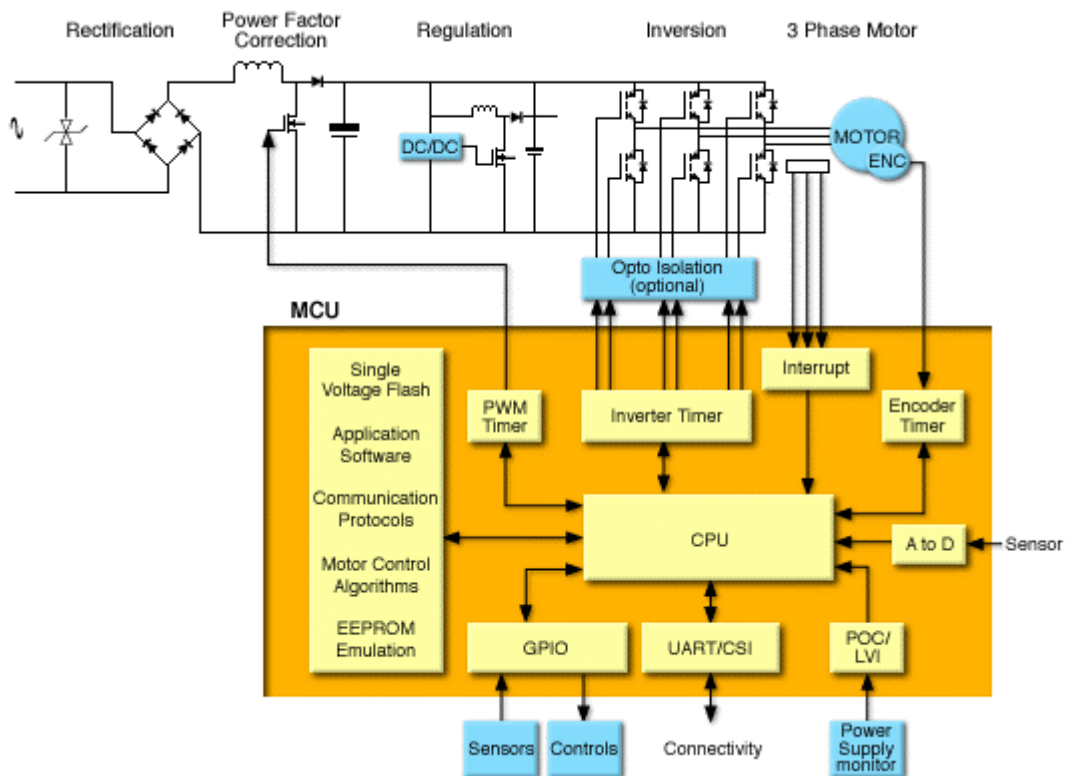


图 (3)